

ECE101-1L – FUNDAMENTALS OF ELECTRONIC CIRCUITS (LAB)

Activity #2: Diode Rectification


Objectives:

- Use a diode to produce half-wave and full-wave pulsating dc from an ac source
- Compare the operation of a full-wave rectifier with that of a half-wave circuit
- Use Multisim and TinkerCAD for the simulations


Procedures:

Part A. Multisim

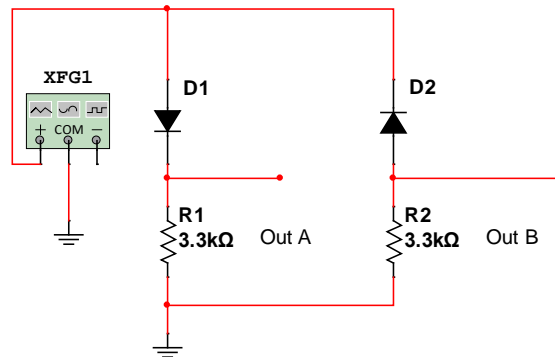1. Open Multisim
2. Create the schematic diagram shown below
(*Function Generator, Resistor, Diode*)



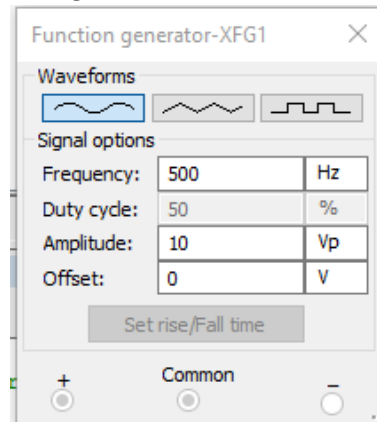3. Change the Function generator Settings




4. Place an Oscilloscope and Probe channel A to Output of the Function Generator and Channel B to the Output A (Across R1) (*You may change the color to identify each waveform and adjust the y-position of each waveform*)
 - a. Screenshot the Output waveform
 - b. Explain the output waveform by comparing the input and output

5. Probe channel A to Output of the Function Generator and Channel B to the Output A (Across R2)
 - a. Screenshot the Output waveform (*You may change the color to identify each waveform*)

b. Explain the output waveform by comparing the input and output

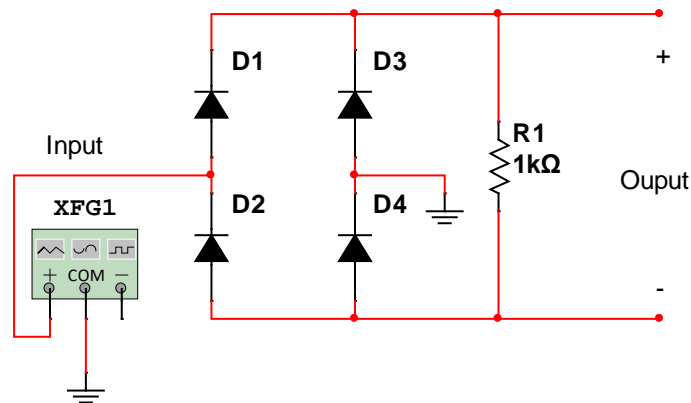6. Create the schematic diagram shown below with same function generator settings from Part A.



7. Place an oscilloscope and Probe Channel A to the Input (Output of the Function Generator), negative probe terminal must be connected to Ground, then probe Channel B to the Output (+) and the negative terminal to the (-) of the Output. (*Change the Colors and Position of waveforms*)

a. Screenshot the Output waveform


b. Explain the output waveform by comparing the input and output

8. Explain how Half-wave Rectifier works (Use Diagram /Figures)

9. Explain how Full-wave Rectifier works (Use Diagram /Figures)


Part B. TinkerCAD

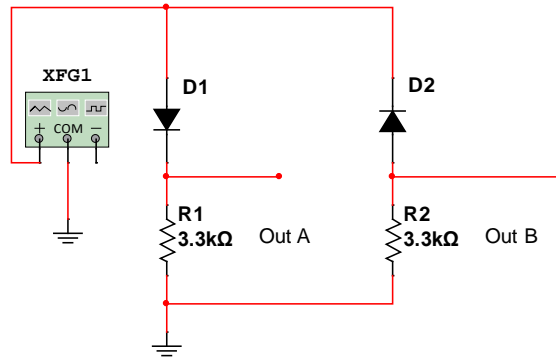1. Create the similar circuit using TinkerCAD
 - a. Screenshot your Breadboard



2. Place Two Oscilloscope (Connected to Output A and Connected to Output B)
 - a. Screenshot the Output waveform of Oscilloscope at Output A
 - b. Screenshot the Output waveform of Oscilloscope at Output B

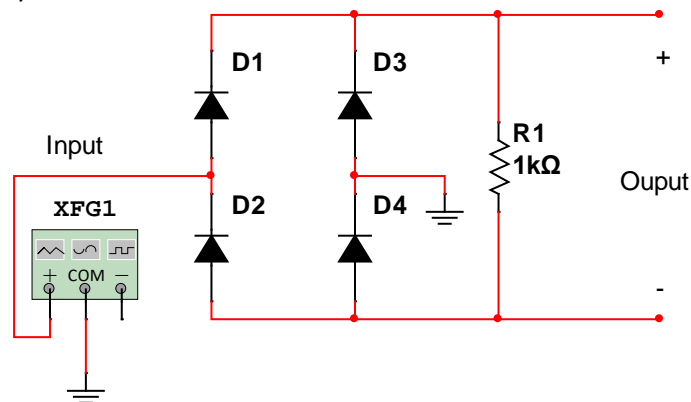3. Create the similar circuit using TinkerCAD
 - a. Screenshot your Breadboard



4. Place Oscilloscope
 - a. Screenshot the Output waveform of Oscilloscope at Output



Discussions:
